

DIGITAL LOGIC DESIGN LAB (EET1211)

LAB II: Examine and analyze the gate level minimization for Boolean function

Siksha 'O' Anusandhan (Deemed to be University), Bhubaneswar

Branch:	Section:	Subgroup No.:
Name	Registration No.	Signature

Marks: ____/10

Remarks:

Teacher's Signature

I. Objective:

1. Construct a circuit for the Boolean function given below using basic gates and verify the truth table.
 - a) $F(A, B, C) = AB + AB'C$
 - b) $F(X, Y, Z) = XY + X'Z + Y'Z$
2. Simplify the following Boolean functions to minimum number of literals and design the circuit using minimum number of basic gates.
 - a) $F(X, Y, Z) = X'Y'Z' + X'YZ' + XY'Z' + XYZ'$
 - b) $F(X, Y, Z) = XYZ' + X'Y + X'Z + YZ$

II. Pre-lab:

For each objective in prelab describe the following points:

- a) Draw the circuit diagram.
- b) Obtain the truth table.

III. LAB:

Components Required:

<u>Sl. No.</u>	<u>Name of the Components</u>	<u>Specification</u>	<u>Quantity</u>
----------------	-------------------------------	----------------------	-----------------

Observation:

IV. Conclusion:

V. POST LAB:

1. Prove the following equation using truth table:
$$(x + y)(x' + z) = xz + x'y$$
2. Draw a circuit that uses only one AND gate and one OR gate to realize the Boolean function

$$F = WXYZ + VXYZ + UXYZ$$