

## HDL code for Flipflop

### D-FF D flip-flop with negative edge-triggering: Source Code

```
library ieee ;
use ieee.std_logic_1164.all;
use work.all;

-----

entity dff is
port (D:    in std_logic;
      CLK:   in std_logic;
      Q,Qb  : out std_logic
);
end dff;

-----

architecture behv of dff is
begin
process (D, CLK)
begin
if (CLK'EVENT AND CLK='0') then    ---this is for data flip-flop, for delay flip-flop use negative edge
    Q <= D;
    Qb <= not D;
end if;
end process;
end behv;
```

### D-FF with negative edge-triggering: Testbench Code

```
library ieee;
use ieee.std_logic_1164.all;

entity dff_TB is          -- entity declaration
end dff_TB;

-----

architecture TB of dff_TB is

    component dff
    Port ( D, CLK: in STD_LOGIC;
          Q, Qb : out STD_LOGIC);
    end component ;
    signal D, CLK, Q, Qb : STD_LOGIC;
    begin
    uut: dff port map(D => D,CLK => CLK,Q => Q,Qb => Qb);

    Clock : process
    begin
    CLK <= '0';
    wait for 10 ns;
```

```

CLK <= '1';
wait for 10 ns;
end process;

```

```

stim : process
begin

```

```

D <= '0';
wait for 40 ns;
D <= '1';
wait for 40 ns;


```

```


end process;
end TB;

```

### RTL SCHEMATIC OF D-FF:

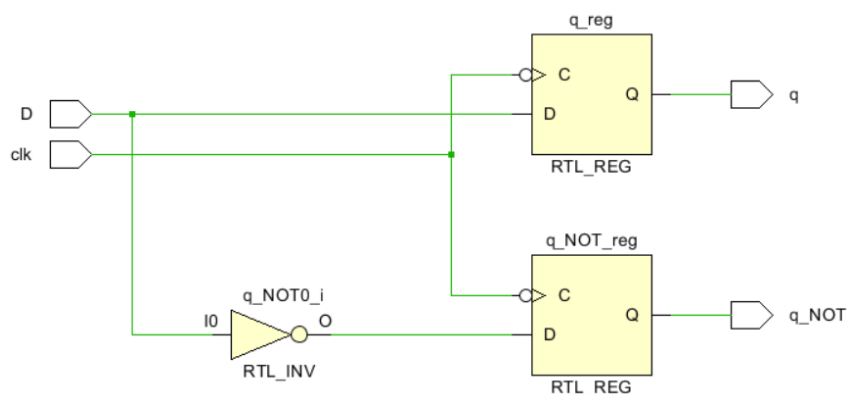

### TESTBENCH WAVEFORM FOR D-FF:

 

### JK flip-flop with active low asynchronous reset and positive edge-triggering:

#### source code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity JKFF_RST is
    port( RST,CLK,J, K: in std_logic;
          Q, Qbar : OUT std_logic);
end JKFF_RST;
architecture behavioral of JKFF_RST is
    signal qn : std_logic;

```

```

begin
process(clk, rst,J,K)

begin
if(rst = '0')then
    qn <= '0';
elsif(clk'event and clk = '1')then
    if(J='0' and K='0')then
        qn <= qn;
    elsif(J='0' and K='1')then
        qn <= '0';
    elsif(J='1' and K='0')then
        qn <= '1';
    elsif(J='1' and K='1')then
        qn <= not qn;
    end if;
end if;

Q <= qn;
Qbar <= not qn;

end process;

end Behavioral;

```

#### **TESTBENCH CODE:**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

entity JK_FF_tb is
-- Port ( );
end JK_FF_tb;

```

```

architecture tB of JK_FF_tb is

```

```

    component JKFF_RST is
    port (RST,CLK, J, K: in std_logic;
        Q, Qbar : out std_logic);
    end component;

```

```

    signal J, K, clk, rst : std_logic;
    signal Q, Qbar : std_logic;

```

```

begin
    uut: JKFF_RST port map(J => J, K => K, clk => clk, rst => rst, Q => Q, Qbar => Qbar);

```

```

    clock: process
    begin

```

```
clk <= '1';  
wait for 10 ns;  
clk <= '0';  
wait for 10 ns;  
end process;
```

```
Force: process  
begin  
J <= '0';  
K <= '0';  
rst <= '0';  
wait for 20 ns;
```

```
J <= '0';  
K <= '1';  
rst <= '0';  
wait for 20 ns;  
J <= '1';  
K <= '0';  
rst <= '1';  
wait for 20 ns;
```


```
J <= '1';  
K <= '1';  
rst <= '1';  
wait for 20 ns;
```

```
J <= '1';  
K <= '1';  
rst <= '0';  
wait for 20 ns;
```



```
J <= '0';  
K <= '0';  
rst <= '0';  
wait for 20 ns;
```

```
J <= '0';  
K <= '0';  
rst <= '1';  
wait for 20 ns;  
end process;  
END tb;
```

 **RTL SCHEMATIC OF JK flip-flop with active low asynchronous reset and positive edge-triggering**



## TESTBENCH WAVEFORM

 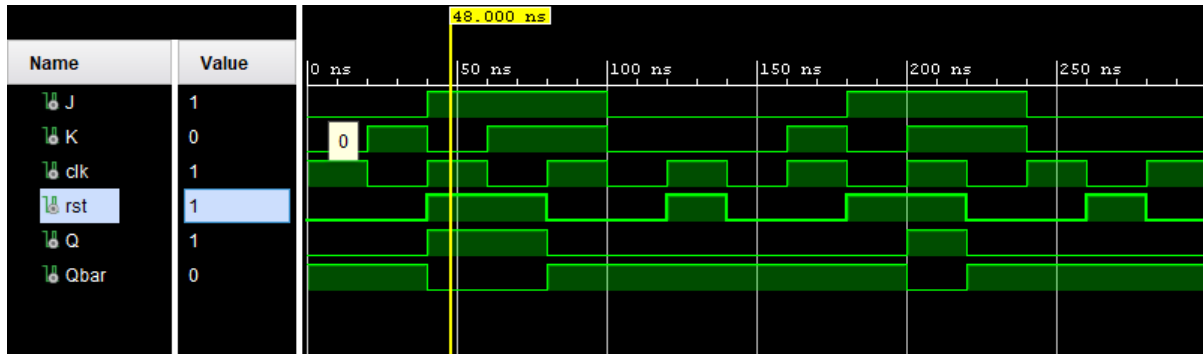

## Obj-3: T-FF with active low asynchronous reset and positive edge-triggering:

### SOURCE CODE:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity T_FF_RST is
    Port ( RES,CLK, T: in STD_LOGIC;
          Q,Q_NOT : BUFFER STD_LOGIC);
end T_FF_RST;

architecture Behavioral of T_FF_RST is
begin
    Q_NOT<= NOT Q;
    PROCESS(T,CLK,RES)
```

```

BEGIN
IF(RES='0') THEN
    Q <='0';
ELSIF (rising_edge(CLK)) THEN
    IF(T='1')THEN
        Q<= NOT Q;
    END IF;
END IF;

END PROCESS;
END Behavioral;

```

#### **TESTBENCH CODE:**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity TFF_tb is
end entity;

architecture tb of TFF_tb is
    component T_FF_RST is
        Port (RES,CLK, T: in STD_LOGIC;
            Q,Q_NOT : BUFFER STD_LOGIC);
    end component;

    signal T,CLK,RES,Q,QB : STD_LOGIC;

    begin
        uut: T_FF_RST port map(RES, CLK, T,Q,QB);

        clock : process
        begin

            CLK <= '0';
            wait for 20 ns;
            CLK <= '1';
            wait for 20 ns;

        end process;

        stim: process
        begin
            RES <= '0';
            T <= '0';
            wait for 20 ns;

```

```

T <= '1';
RES <= '1';
wait for 20 ns;

```

```

RES <= '1';
T <= '0';
wait for 20 ns;
RES <= '1';
T <= '1';
wait for 20 ns;


```

```

end process;
end tb;


```
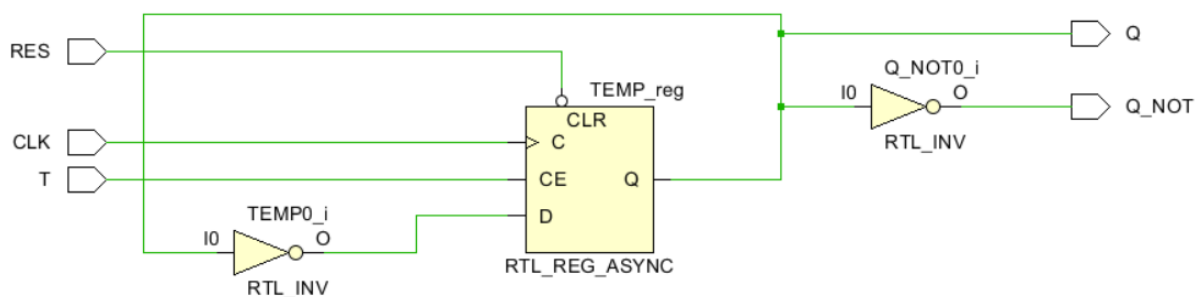
### RTL SCHEMATIC OF T-FF with active low asynchronous reset and positive edge-triggering



### TESTBENCH WAVEFORM

 1. Cursor point indicates CLK=1, RST=1, T=1, Q(t)=0, SO, Q(t+1)=1



2. Cursor point indicates CLK=1, RST=1, T=1, Qt =1, So, Q(T+1)=0

