

# CONTENTS


S. No.	Name Of The Experiment	Date of Experiment	Page No.	Signature
1	<del>Obj</del> LAB I : objective 1 :- Investigation of logic behavior of various gates	09/10/23	1-6	
2	Objective 2 :- Using a single 7400 IC, connect a circuit that produces:	16/10/23	1-6	<del>He</del> 06/11/2023
3	LAB-II : Objective 1 :- Construct a circuit using basic gates : $F = AB + AB'C$	06/11/23	7-13	<del>He</del> 06/11/2023
4	Objective 2 :- construct a circuit for : $F = XY + X'Z + YZ$ Objective 3 :- Construct circuit for : $F = (X'Y + YZ)' + YZ$	06/11/23	7-13	<del>He</del>
5	LAB 3 : Objective 1 Objective 2 (a), 2b Objective 3	13/11/23	14-19	<del>He</del>
6	LAB 4 : Objective 1, Objective 2 Objective 3	13/11/23	20-25	<del>He</del>
7	LAB 5 : Objective 1 Objective 2, Objective 3	20/11/23	26-31	<del>He</del>
8	LAB 6 : Objective 1, Objective 2, Objective 3	20/11/23	32-36	<del>He</del>
9	LAB 7 : 3 Objectives	07/01/24	37-46	<del>He</del>
10	LAB 8 : 3 Objectives	15/01/24	47-55	<del>He</del>
11	LAB 9 : 3 Objectives	15/01/24	56-64	<del>He</del>

# DIGITAL LOGIC DESIGN LAB (EET1211)

---

## LAB I: Examine the Operation of Logic Gates

Siksha 'O' Anusandhan Deemed to be University, Bhubaneswar

Branch:	Section:	Sub Group Number:
Name	Registration No.	Signature
RAJ ARYAN	2241001092	

Marks: 09 /10

Remarks:


  
Teacher's Signature



## II. PRE-LAB


1. 7400 Quad 2-input NAND gate :

A	B	$F = (A \cdot B)'$
0	0	1
0	1	1
1	0	1
1	1	0

 


2. 7402 Quad 2-input NOR gates :

A	B	$F = (A + B)'$
0	0	1
0	1	0
1	0	0
1	1	0

 


3. 7404 hex inverter :

A	$F = A'$
0	1
1	0

 


4. 7408 Quad 2-input AND gates:

A	B	$F = (A \cdot B)$
0	0	0
0	1	0
1	0	0
1	1	1

 


5. 7432 Quad 2-input OR gates:

A	B	$F = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

 

6. 7486 Quad 2-input XOR gates:


A	B	$F = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

 

7. (a) An inverter:

A	$A'$
0	1
1	0

NOT:

 




(b) A 2-input AND :

A	B	A·B
0	0	0
0	1	0
1	0	0
1	1	1


AND :

 

(c) A 2-input OR :

A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1


OR :

 

(d) A 2-input XOR :

A	B	A⊕B
0	0	0
0	1	1
1	0	1
1	1	0

XOR :

 

III. LAB :

Components Required :-

Objective 2

Sl. No.	Components Name (Description)	Quantity
1	7400 IC (NAND)	1
2	Wires	As required



## Objective 1

Sl.No.	Components (Description)	Quantity
1	Wires	As required
2	7400 IC (NAND)	1
3	7432 IC (OR)	1
4	7486 IC (XOR)	1
5	7408 IC (AND)	1
6	7404 IC (NOT)	1
7	7402 IC (NOR)	1

## Observation Table :-

### Objective 1

(a) 7400 IC (NAND) :

I/P	O/P	Status
1, 2	3	Working
4, 5	6	Working
9, 10	8	Working
12, 13	11	Working

(b) 7402 IC (NOR) :

I/P	O/P	Status
2, 3	1	Working
5, 6	4	Working
9, 9	10	Working
11, 12	13	Working

(c) 7404 IC (NOT) :

I/P	O/P	Status
1	2	Working
3	4	Working
5	6	Working
9	8	Working
11	10	Working
13	12	Working

(d) 7408 IC (AND) :

I/P	O/P	Status
2, 1	3	Working
5, 4	6	Working
10, 9	8	Working
13, 12	11	Working



(e) 7432 IC (OR) :

I/P	O/P	Status
1, 2	3	Working
4, 5	6	Working
9, 10	8	Working
12, 13	11	Working

(f) 7486 IC (XOR) :

I/P	O/P	Status
1, 2	3	Working
4, 5	6	Working
9, 10	8	Working
12, 13	11	Working

## Objective 2

(a) An inverter (NOT) :

A	Y	Status
0	1	Working
1	0	Working

(b) A 2-input AND :

A	B	Y	Status
0	0	0	Working
0	1	0	Working
1	0	0	Working
1	1	1	Working

(c) A 2-input OR :

A	B	Y	Status
0	0	0	Working
0	1	1	Working
1	0	1	Working
1	1	1	Working

(d) A 2-input XOR :

A	B	Y	Status
0	0	0	Working
0	1	1	Working
1	0	1	Working
<del>1</del>	<del>1</del>	<del>0</del>	Working

## Conclusion :-

### Objective 1

We have concluded that all pins of given ICs are working perfectly.



## Objective 2

We have concluded that NAND is a universal gate because we are able to produce an inverter, AND, OR and an XOR gate using one 7400 IC.

## IV. POST LAB :

1. What is the voltage range for operation of digital circuits?  
→ The voltage range for operation of digital circuits is (0-5) volts.
2. What is the significance of ground and  $V_{cc}$  connection?  
→  $V_{cc}$  is the power input for a device, it provides the voltage to the circuit generally higher than the ground.
3. Which gates are known as the universal gates & why?  
→ NAND & NOR gates are the ~~the~~ universal gates because we can construct any gates using this.
4. What is the min<sup>m</sup> no. of NAND gates used to realize an XOR gate?  
→ <sup>At least</sup> 4 NAND gates are required to realize an XOR gate.

*22/11/25*